



YCCE, Nagpur



MGI

DAC interfacing with 8051

Dr. P. T. Karule

Professor


Department of Electronics Engineering

Yeshwantrao Chavan College of Engineering, Nagpur (M. S.)

Email: ptkarule@ycce.edu

Website: www.ycce.edu

Interfacing 8 bit DAC (Unipolar O/P)

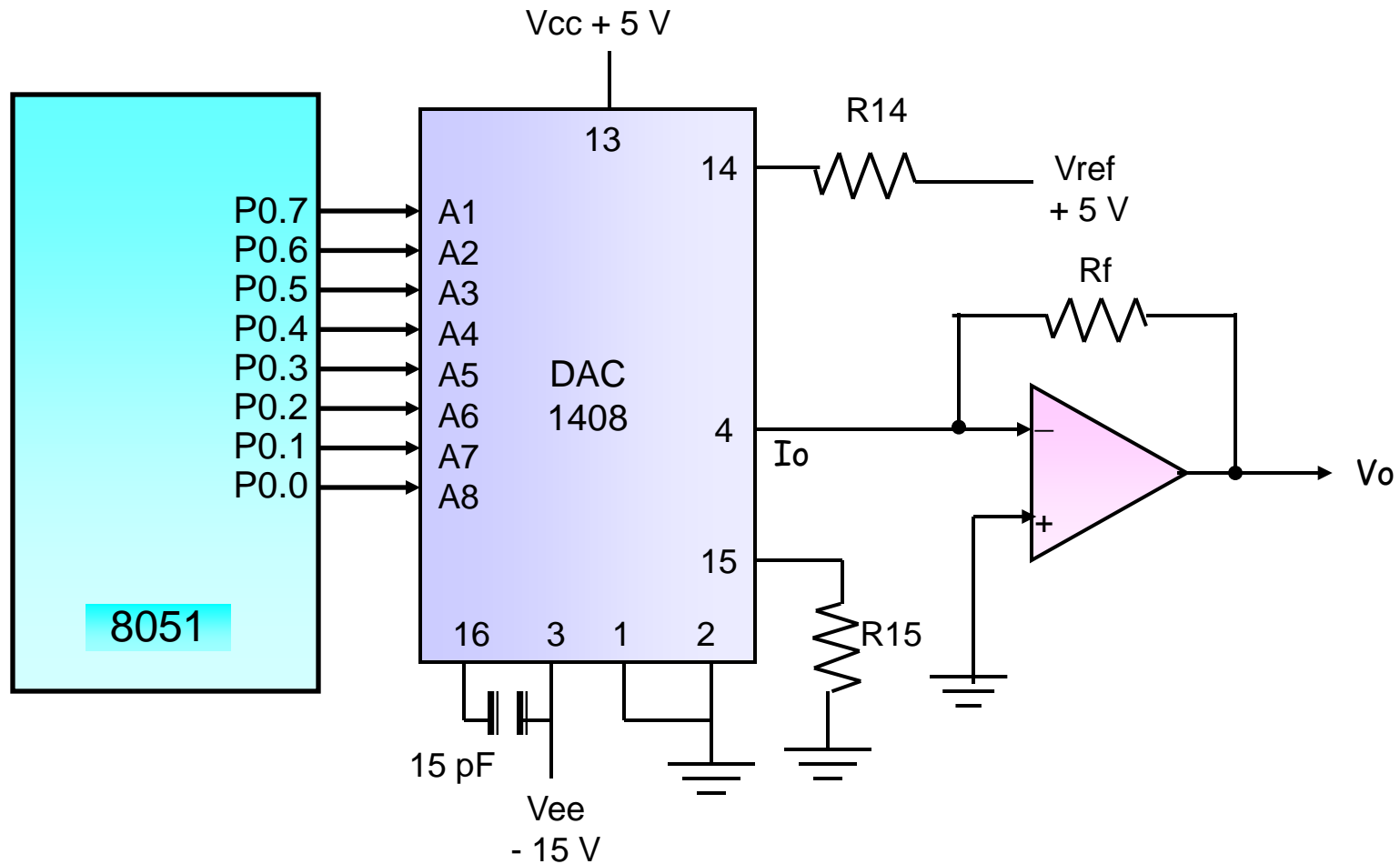

$$I_o = V_{ref}/R_{14} * (A_1/2 + A_2/4 + A_3/8 + A_4/16 + A_5/32 + A_6/64 + A_7/128 + A_8/256)$$

$$V_o = I_o * R_f$$

Interfacing 8 bit DAC (cont..)

$I_{ref} = V_{ref} / R_{14} = \text{Maximum output current}$

Suppose $V_{ref} = 5 \text{ V}$, $R_{14} = 2.5 \text{ K}$ then $I_{ref} = 5 / 2.5 = 2 \text{ mA}$

$I_o (\text{max}) = 2 \text{ mA}$, $V_o = I_o * R_f$

If $R_f = 2.5 \text{ K}$, then $V_o (\text{max}) = 2 \text{ mA} * 2.5 \text{ K} = 5 \text{ V}$

If $R_f = 5 \text{ K}$, then $V_o (\text{max}) = 2 \text{ mA} * 5 \text{ K} = 10 \text{ V}$

e.g. If binary input $A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 = 11111111$, then

$$I_o = 5/2.5\text{K} * (1/2 + 1/4 + 1/8 + 1/16 + 1/32 + 1/64 + 1/128 + 1/256)$$

$$I_o = 5/2.5\text{K} * (255/256) \sim 2 \text{ mA}$$

e.g. If binary input $A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 = 10000000$, then

$$I_o = 5/2.5\text{K} * (1/2 + 0/4 + 0/8 + 0/16 + 0/32 + 0/64 + 0/128 + 0/256)$$

$$I_o = 5/2.5\text{K} * (1/2) \sim 1 \text{ mA}$$

e.g. If binary input $A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 = 00000011$, then

$$I_o = 5/2.5\text{K} * (0/2 + 0/4 + 0/8 + 0/16 + 0/32 + 0/64 + 1/128 + 1/256)$$

$$I_o = 5/2.5\text{K} * (3/256) \sim 0.02343 \text{ mA}$$


e.g. If binary input $A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 = 00000000$, then

$$I_o = 5/2.5\text{K} * (0/2 + 0/4 + 0/8 + 0/16 + 0/32 + 0/64 + 0/128 + 0/256)$$

$$I_o = 5/2.5\text{K} * (0) \sim 0 \text{ mA}$$


DAC input / output table (Unipolar)

Input		$R_f = 2.5 \text{ K}$	Output
Binary	I_o	$V_o = I_o * R_f$	V_o
00H	0 mA	$0 * 2.5$	0 V
01H	0.0078 mA	$0.0078 * 2.5$	19.5 mV
03H	0.02343 mA	$0.02343 * 2.5$	58.5 mV
7FH	1 mA	$1 * 2.5$	2.5 V
FFH	2 mA	$2 * 2.5$	5 V

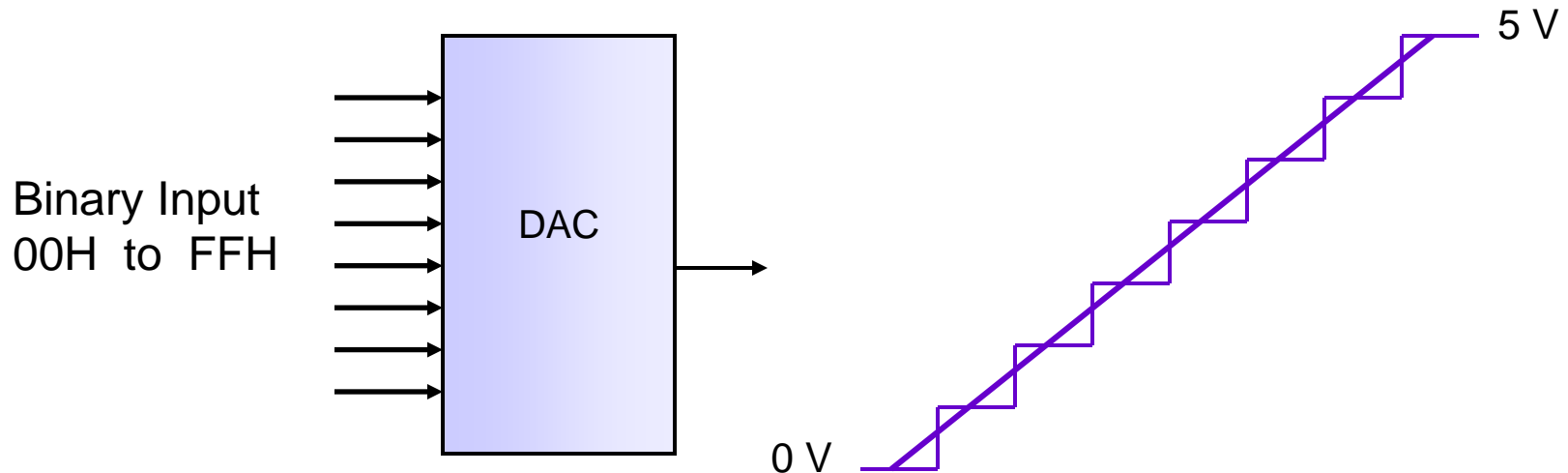

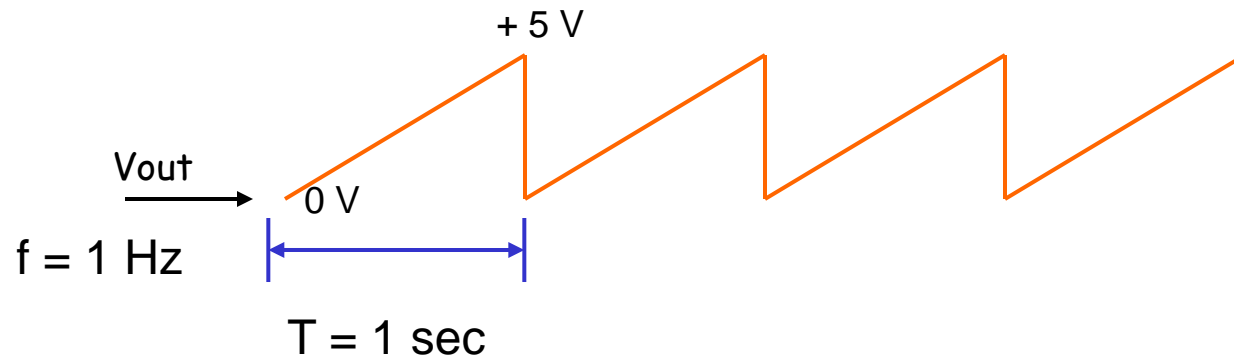Problem #1

Q. Write program to generate saw-tooth wave using DAC as shown.




$$T = 1/f = 1 \text{ sec}$$

0 V to 5 V there are 256 steps (8 bit input)

$$\begin{aligned} \text{Hence Delay per step} &= 1 \text{ sec} / 256 = 1000 \text{ msec} / 256 \\ &= 3.906 \text{ msec} \end{aligned}$$

Problem #1...

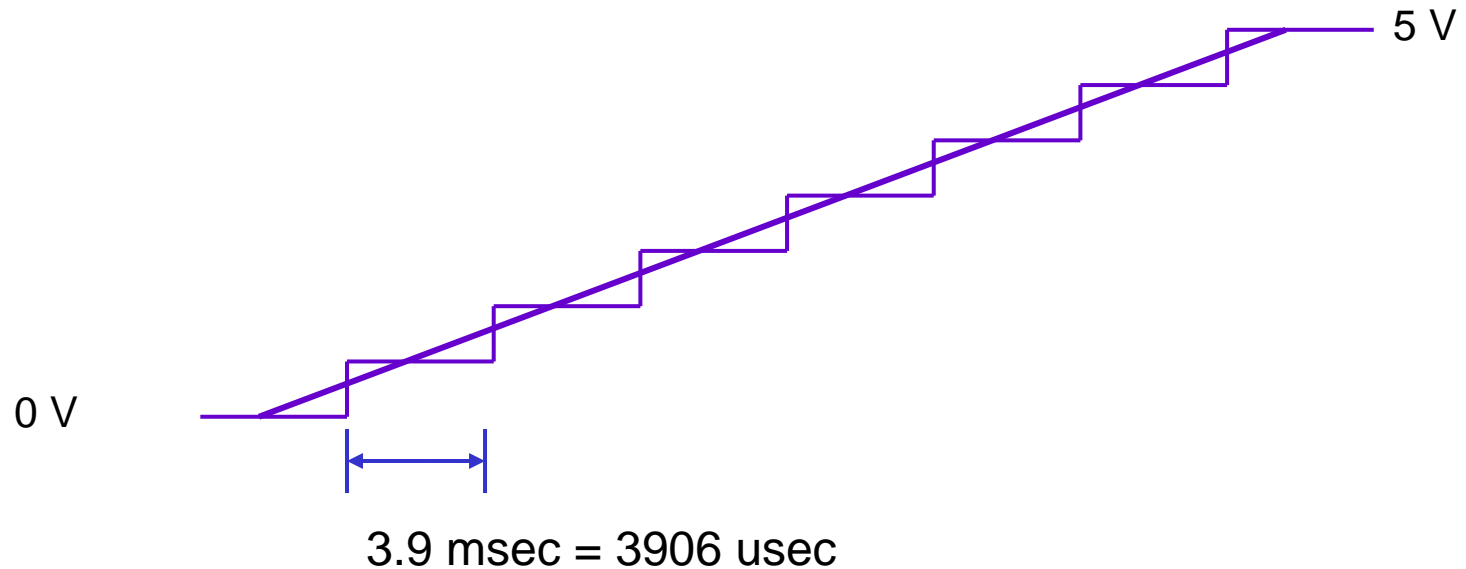

Delay Program **Calculation of N**

$$\begin{aligned}\text{No. of m/c cycles} &= 1 + N1 * (1 + 2 * N2 + 2) \\ &= 3906\end{aligned}$$

Assume $N1 = 8$, then $N2 = ?$

$$1 + 8 * (1 + 2 * N2 + 2) = 3906$$

$$N2 = 243$$

Problem #1...

■ Program:


```
        MOV A, #00H           ; Clear Accumulator
LOOP:   MOV P0, A             ; Send data to DAC
        INC A                 ; Increment Acc
        ACALL DELAY          ; Delay per step
        SJMP LOOP            ; Repeat
```

; Subroutine for Delay of 3.906 msec

```
DELAY:  MOV R1, #08H         ; N1=8
L2:     MOV R2, #F3H         ; N2=243
L1:     DJNZ R2, L1
        DJNZ R1, L2
        RET
```

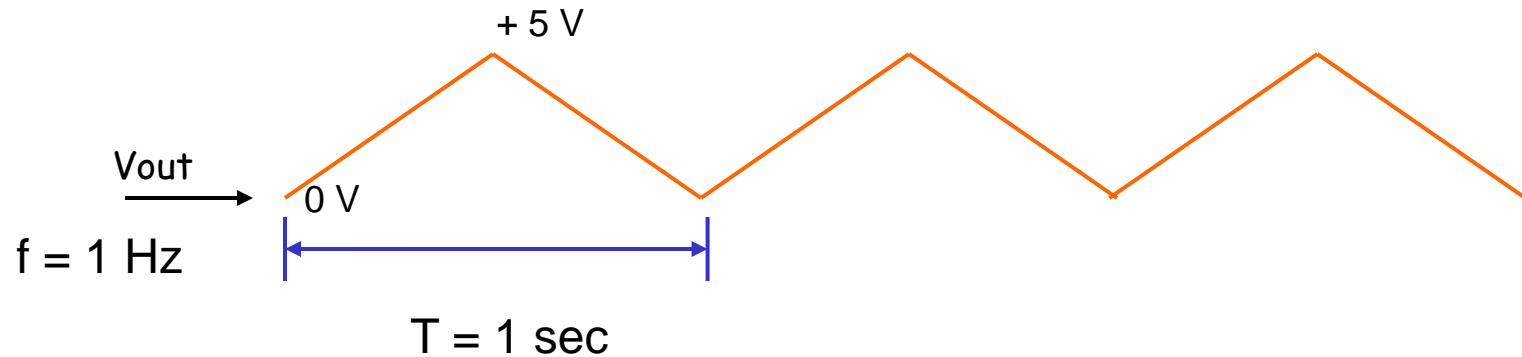Problem # 2

Q. Write program to generate triangular wave using DAC as shown.




$$T = 1/f = 1 \text{ sec}$$

0 V to 5 V & then 5 V to 0 V there are 256 + 256 steps (8 bit input)

$$\begin{aligned} \text{Hence Delay per step} &= 1 \text{ sec} / 512 = 1000 \text{ msec} / 512 \\ &= 1.953 \text{ msec} \end{aligned}$$

Problem #2...

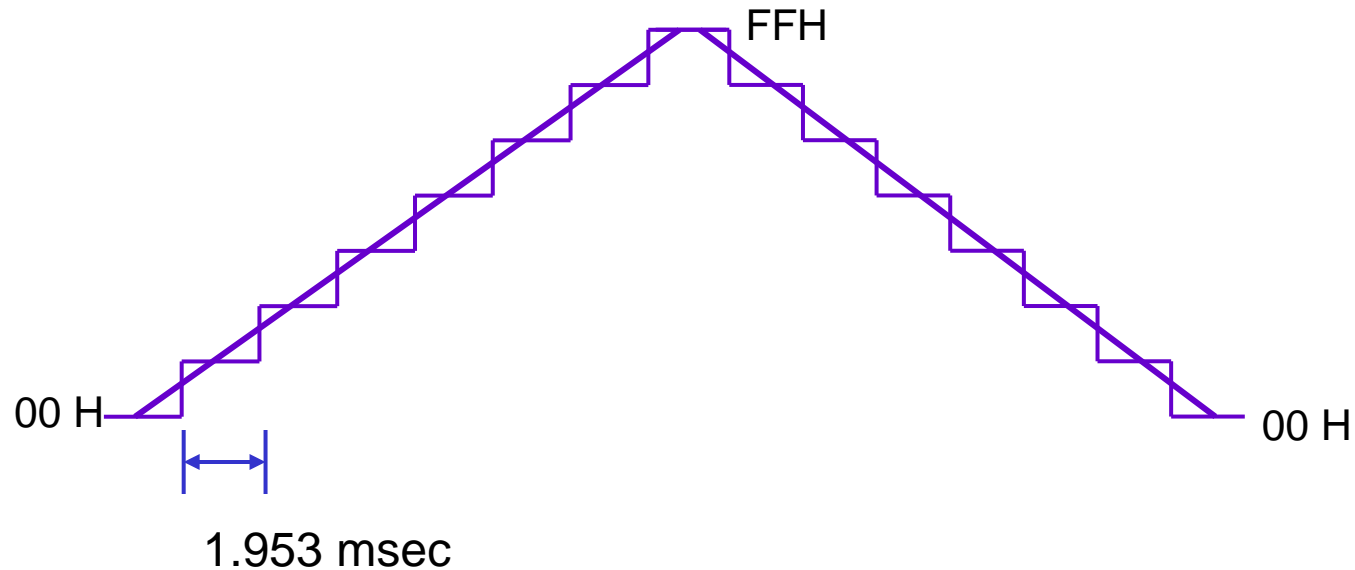

Delay Program **Calculation of N**

$$\begin{aligned}\text{No. of m/c cycles} &= 1 + N1 * (1 + 2 * N2 + 2) \\ &= 1953\end{aligned}$$

Assume $N1 = 4$, then $N2 = ?$

$$1 + 4 * (1 + 2 * N2 + 2) = 1953$$

$$N2 = 243$$

Problem #2...


■ Program:

```
        MOV A, #00H           ; Clear Accumulator
L3:     MOV P0, A             ; Send data to DAC
        INC A                 ; Increment Acc
        ACALL DELAY          ; Delay per step
        CJNE A, #FFH, L3     ; Repeat if not FFH
L4:     MOV P0, A             ; Send data to DAC
        DEC A                 ; Decrement Acc
        ACALL DELAY          ; Delay per step
        CJNE A, #00H, L4     ; Repeat if not 00H
        SJMP L3
```

; Subroutine for Delay of 1.953 msec

```
DELAY: MOV R1, #04H          ; N1=4
L2:     MOV R2, #F3H          ; N2=243
L1:     DJNZ R2, L1
        DJNZ R1, L2
        RET
```

Interfacing 8 bit DAC (Bipolar O/P)

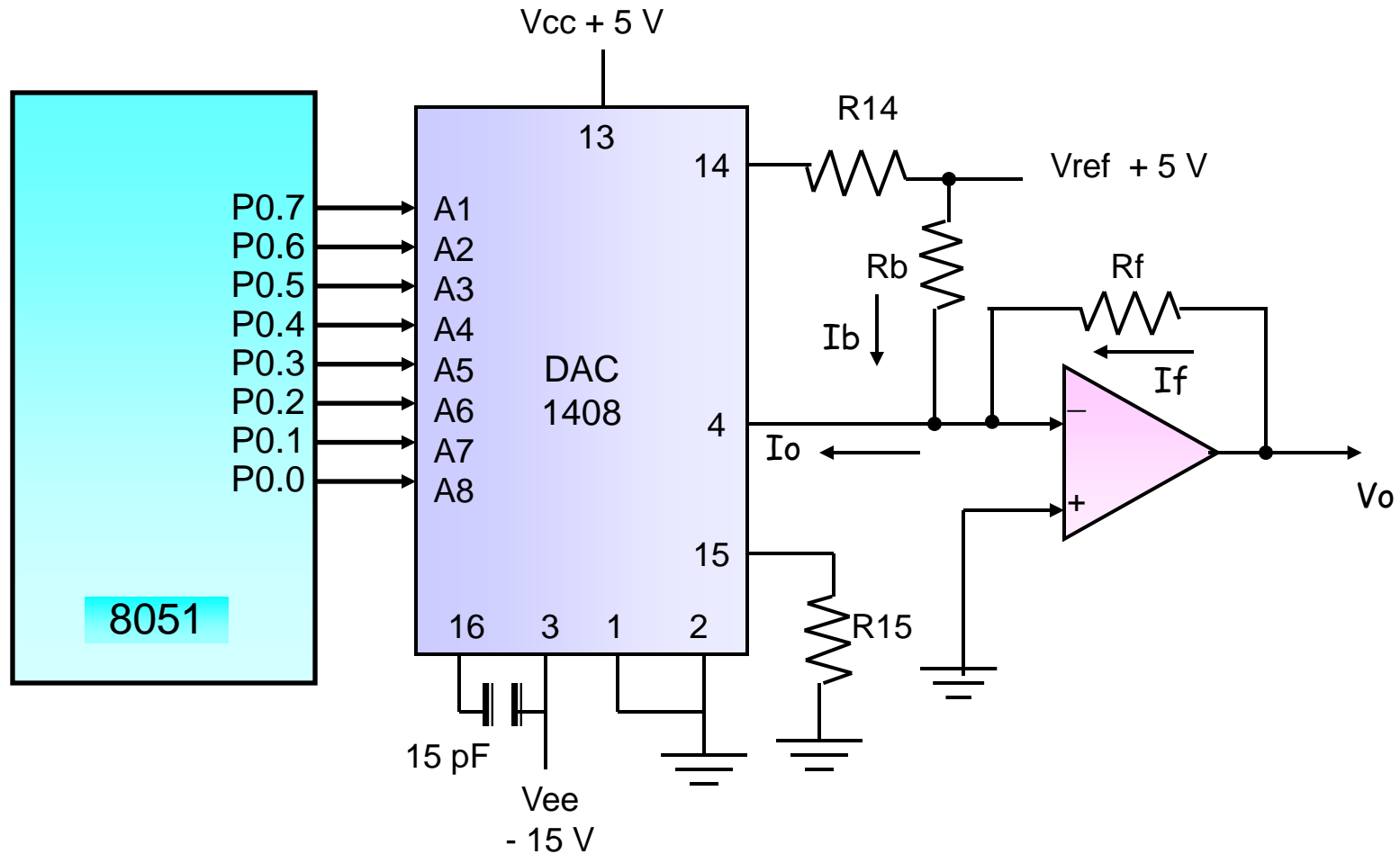

$$I_o = V_{ref}/R_{14} * (A_1/2 + A_2/4 + A_3/8 + A_4/16 + A_5/32 + A_6/64 + A_7/128 + A_8/256)$$

$$I_o = I_f + I_b, \quad I_f = I_o - I_b, \quad V_o = I_f * R_f, \quad V_o = (I_o - I_b) * R_f$$

DAC input / output table (Bipolar)

$I_{ref} = V_{ref} / R_{14} = \text{Maximum output current}$

Suppose $V_{ref} = 5 \text{ V}$, $R_{14} = 2.5 \text{ K}$ then $I_{ref} = 5 / 2.5 = 2 \text{ mA}$

$I_o (\text{max}) = 2 \text{ mA}$

$I_b = V_{ref} / R_b = \text{Bias current}$

Suppose $V_{ref} = 5 \text{ V}$, $R_b = 5 \text{ K}$ then $I_b = 5 / 5 = 1 \text{ mA}$

$I_f = I_o - I_b = I_o - 1 \text{ mA}$

$V_o = (I_o - 1 \text{ mA}) * R_f$

Input		I_f	$R_f = 2.5 \text{ K}$	Output
Binary	I_o	$I_f = I_o - 1 \text{ mA}$	$V_o = I_o * R_f$	V_o
00H	0 mA	- 1 mA	-1 * 2.5	-2.5 V
01H	0.0078 mA	- 0.992 mA	-0.992 * 2.5	- 2.48 V
03H	0.02343 mA	- 0.976 mA	- 0.976 * 2.5	- 2.44 V
7FH	1 mA	0 mA	0 * 2.5	0 V
FFH	2 mA	+ 1 mA	1 * 2.5	+ 2.5 V

Thank You!!